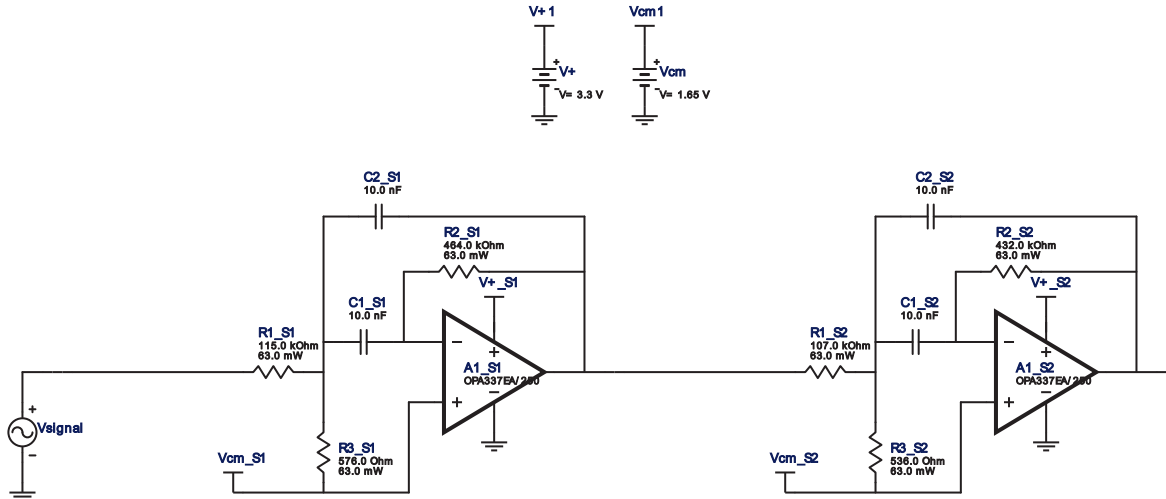


**WEBENCH<sup>®</sup> Design Report**

 Design : 3612920/21 OPA337EA/250  
 Bandpass, Multiple Feedback, Butterworth

**Electrical BOM**

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	A1_S1	Texas Instruments	OPA337EA/250	GbwTyp= 3.0 MHz VccMin= 2.5 V VccMax= 5.5 V	1	\$0.50	MSOP 0 mm <sup>2</sup>
2.	A1_S2	Texas Instruments	OPA337EA/250	GbwTyp= 3.0 MHz VccMin= 2.5 V VccMax= 5.5 V	1	\$0.50	MSOP 0 mm <sup>2</sup>
3.	C1_S1	AVX	06033A102FAT2A Series= C0G/NP0	Cap= 10.0 nF VDC= 25.0 V Tolerance= 1.0 %	1	\$0.14	0603 5 mm <sup>2</sup>
4.	C1_S2	AVX	06033A102FAT2A Series= C0G/NP0	Cap= 10.0 nF VDC= 25.0 V Tolerance= 1.0 %	1	\$0.14	0603 5 mm <sup>2</sup>
5.	C2_S1	AVX	06033A102FAT2A Series= C0G/NP0	Cap= 10.0 nF VDC= 25.0 V Tolerance= 1.0 %	1	\$0.14	0603 5 mm <sup>2</sup>
6.	C2_S2	AVX	06033A102FAT2A Series= C0G/NP0	Cap= 10.0 nF VDC= 25.0 V Tolerance= 1.0 %	1	\$0.14	0603 5 mm <sup>2</sup>
7.	R1_S1	Vishay-Dale	CRCW0402115KFKED Series= CRCW..e3	Res= 115.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm <sup>2</sup>
8.	R1_S2	Vishay-Dale	CRCW0402107KFKED Series= CRCW..e3	Res= 107.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm <sup>2</sup>
9.	R2_S1	Vishay-Dale	CRCW0402464KFKED Series= CRCW..e3	Res= 464.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm <sup>2</sup>
10.	R2_S2	Vishay-Dale	CRCW0402432KFKED Series= CRCW..e3	Res= 432.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm <sup>2</sup>
11.	R3_S1	Vishay-Dale	CRCW0402576RFKED Series= CRCW..e3	Res= 576.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm <sup>2</sup>

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
12.	R3_S2	Vishay-Dale	CRCW0402536RFKED Series= CRCW..e3	Res= 536.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm <sup>2</sup>

## Design Inputs


#	Name	Value	Description
1.	FilterType	Bandpass	
2.	FilterResponse	Butterworth	
3.	FilterOrder	4.0	
4.	FilterTopology	Multiple_Feedback	
5.	NumberOfStages	2.0	
6.	CenterFrequency	1,000.0	
7.	StopbandAttenuation	-10.0	
8.	PassbandBandwidth	100.0	
9.	StopbandBandwidth	200.0	
10.	Gain	2.0	
11.	SingleSupply	3.3	Power supply(s) to active chips
12.	ResistorTolerance	E96	Resistor series - 1% Passive resistor tolerance
13.	CapacitorTolerance	E96	Capacitor series - 1% Passive capacitance tolerance
14.	SeedCapacitance	10.0 n	Seed Capacitance to start design of filter

## Design Assistance

1. **OPA337EA/250** Product Folder : <http://www.ti.com//product/OPA337> : contains the data sheet and other resources.
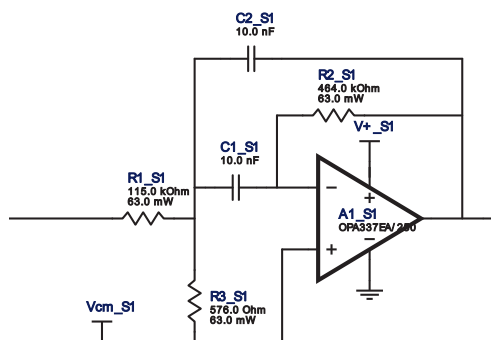
## Filter Stage :1

Cutoff Frequency 965.248 Hz  
 Min GBW Req'd 1.931 MHz  
 Stage Gain 1.414 V/V  
 Stage Q 14.151  
 Stage Topology Multiple\_Feedback




## Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	A1_S1	Texas Instruments	OPA337EA/250	GbwTyp= 3.0 MHz VccMin= 2.5 V VccMax= 5.5 V	1	\$0.50	MSOP 0 mm <sup>2</sup>
2.	C1_S1	AVX	06033A102FAT2A Series= C0G/NP0	Cap= 10.0 nF VDC= 25.0 V Tolerance= 1.0 %	1	\$0.14	0603 5 mm <sup>2</sup>
3.	C2_S1	AVX	06033A102FAT2A Series= C0G/NP0	Cap= 10.0 nF VDC= 25.0 V Tolerance= 1.0 %	1	\$0.14	0603 5 mm <sup>2</sup>
4.	R1_S1	Vishay-Dale	CRCW0402115KFKED Series= CRCW..e3	Res= 115.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm <sup>2</sup>
5.	R2_S1	Vishay-Dale	CRCW0402464KFKED Series= CRCW..e3	Res= 464.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm <sup>2</sup>
6.	R3_S1	Vishay-Dale	CRCW0402576RFBKED Series= CRCW..e3	Res= 576.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm <sup>2</sup>
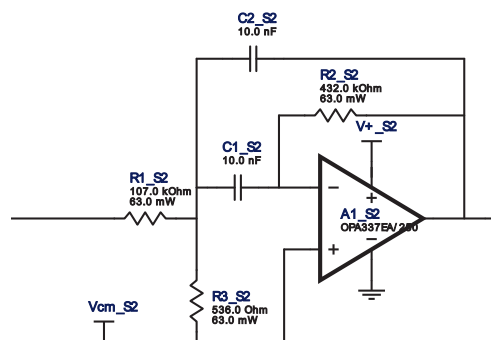
## Filter Stage :2

Cutoff Frequency 1.036 kHz  
 Min GBW Req'd 2.073 MHz  
 Stage Gain 1.414 V/V  
 Stage Q 14.151  
 Stage Topology Multiple\_Feedback



### Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	A1_S2	Texas Instruments	OPA337EA/250	GbwTyp= 3.0 MHz VccMin= 2.5 V VccMax= 5.5 V	1	\$0.50	MSOP 0 mm <sup>2</sup>
2.	C1_S2	AVX	06033A102FAT2A Series= C0G/NP0	Cap= 10.0 nF VDC= 25.0 V Tolerance= 1.0 %	1	\$0.14	0603 5 mm <sup>2</sup>
3.	C2_S2	AVX	06033A102FAT2A Series= C0G/NP0	Cap= 10.0 nF VDC= 25.0 V Tolerance= 1.0 %	1	\$0.14	0603 5 mm <sup>2</sup>
4.	R1_S2	Vishay-Dale	CRCW0402107KFKED Series= CRCW..e3	Res= 107.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm <sup>2</sup>
5.	R2_S2	Vishay-Dale	CRCW0402432KFKED Series= CRCW..e3	Res= 432.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm <sup>2</sup>

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
6.	R3_S2	Vishay-Dale	CRCW0402536RFKED Series= CRCW..e3	Res= 536.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm <sup>2</sup>

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

**You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.**

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).